Data Pin = Port A Pin 0 Store Pin = Port A Pin 1 Refresh Pin = Port A Pin 4 DHT22 Pin = Port B Pin 0

8-Bit shift register https://pdf1.alldatasheet.com/datasheet-pdf/view/797421/TI1/SN74HC595N.html

7-seg-display https://pdf1.alldatasheet.com/datasheet-pdf/view/1134416/ETC2/5611AH.html GND 3 und 8 (eine Verbindung reicht)

Verbindungen 8-Bit shift register -> 7-seg-display  $qA \rightarrow A$  (Pin 7)  $qB \rightarrow B$  (Pin 6)  $qC \rightarrow C$  (Pin 4)  $qD \rightarrow D$  (Pin 2)  $qE \rightarrow E$  (Pin 1)  $qF \rightarrow F$  (Pin 9)  $qG \rightarrow G$  (Pin 10)  $qH \rightarrow H$  (Pin 5)

qH' -> ser (nächster display)